

Lab 5 EC413

Members: Pree Simphliphon, Rayan Syed

Components of Lab + Explanation:

SLT:

Since SLT is R-type we reused the instruction used for the add/xor etc. in the control module

In the ALU_control module we made sure that the instruction for SLT would choose the ALU function (function 6):

```
        else if (instruction == 6'h2a) //slt
control: func = 4'd6;
```

```
        else if (func == 4'd6)
ALU_control: out = a<b;
```

We implemented this just like the prelab's xor

Jump:

For jump we had to add a jump register output for control, to be passed to more modules in the overall cpu. The rest of this code chunk is the same as that for branch (in control.v)

```

    else if (instruction == 6'b000010) begin //jump
        ALUOp = 2'b01;
        MemRead = 1'b0;
        MemtoReg = 1'b0;
        RegDst = 1'b0;
        Branch = 1'b1;
        ALUSrc = 1'b0;
        MemWrite = 1'b0;
        RegWrite = 1'b0;
        jump = 1;
    end

```

This new code was added as per the discussion slides for the lab; this let us successfully implement jump:

```

//for jump
wire [31:0] jumpaddress;
shift_left_2 #(32) Shift_Left_Two2 (instruction[25:0], jumpaddress[27:0]);
assign jumpaddress = {PC_plus_4 [31:28], jumpaddress[27:0]};
mux #(32) jump_MUX (jump, PC_in1, jumpaddress, PC_in);

wire [31:0]

```

ADDI, ORI, LUI:

For these 3 immediate functions we simply had to make the first 6 instruction digits trigger the I-type signal in control to be dealt with in ALU_control. The rest of the code chunk is the same as R-type (except ALUSrc)

```

    else if (instruction == 6'b001000 || instruction == 6'b001101 || instruction == 6'b001111) begin //IType
        ALUOp = 2'b01;
        MemRead = 1'b0;
        MemtoReg = 1'b0;
        RegDst = 1'b0; // select R2 as written register
        Branch = 1'b0;
        ALUSrc = 1'b1; // choose immediate as R3
        MemWrite = 1'b0;
        RegWrite = 1'b1;
        jump = 0;
    end
end

```

The functions simply called the same ALU functions as add/or for addi/ori, but for lui we added a 7th function that simply shifted left 16 bits (will not attach screenshot since so simple):

```
...
if (instruction2 == 6'h08)
    func = 4'd0;
//ori
else if(instruction2==6'h0d)
    func = 4'd3;

//lui
else if(instruction2==6'h0f)
    func= 4'd7;

```

BNE:

While doing BNE, we also reimplemented BEQ. We essentially just added two functions to the ALU that would deal with beq and bne. If beq, the zero_flag would be 0; if if bne, the zero_flag would be 1. To do this, we increased the size of the func to 4 bits rather than 3 so we could have a function 9/10 for beq and bne respectively.

BEQ and BNE functions - this code falls under the ALU_control block:

```
//beq
else if(instruction2== 6'h04)
    func = 4'd8;

//bne
else if (instruction2 == 6'h05)
    func = 4'd9;
...

```

Testbench:


We updated the testbench to include test cases for all the new functions.

We pulled out PC_out to see where the current instruction was.

Here is the relevant waveform:


> instruction_initialize_data[31:0]	1000ffff	00000000	1000ffff
> instruction_initialize_address[31:0]	00000044	00000000	00000044
> register_file[0:31][31:0]	00000000,fffffc5,00000000	00000000,0000000a,00000014,0000001e,00000028,00...	00000000,fffffc5,0000000e,00000014,000000...
> [0][31:0]	00000000	00000000	00000000
> [1][31:0]	fffffc5	0000000a	fffffc5
> [2][31:0]	0000000e	00000014	0000000e
> [3][31:0]	00000014	0000001e	00000014
> [4][31:0]	00000028	00000028	00000028
> [5][31:0]	00000032	00000032	00000032
> [6][31:0]	0000003c	0000003c	0000003c
> [7][31:0]	0000003e	00000046	0000003e
> [8][31:0]	00000000	00000050	00000000
> [9][31:0]	0000005a	0000005a	0000005a
> [10][31:0]	00000064	00000064	00000064
> [11][31:0]	0000006e	0000006e	aaaa0000
> [12][31:0]	0000005a	00000078	0000005a
> [13][31:0]	00000082	00000082	00000082
> [14][31:0]	0000008c	0000008c	00000088
> [15][31:0]	00000096	00000096	00000096
> [16][31:0]	000000a0	000000a0	00000096
> [17][31:0]	000000aa	000000aa	000000aa
> [18][31:0]	000000b4	000000b4	000000b4
> [19][31:0]	000000be	000000be	00000001
> [20][31:0]	000000c8	000000c8	000000c8
> [21][31:0]	000000d2	000000d2	000000d2
> [22][31:0]	000000dc	000000dc	000000dc
> [23][31:0]	000000e6	000000e6	000000e6
> [24][31:0]	000000f0	000000f0	000000f0
> [25][31:0]	000000fa	000000fa	000000fa
> [26][31:0]	00000104	00000104	00000104
> [27][31:0]	0000010e	0000010e	0000010e
> [28][31:0]	00000118	00000118	00000118
> [29][31:0]	00000122	00000122	00000122
> [30][31:0]	0000012c	0000012c	0000012c
> [31][31:0]	00000136	00000136	00000136
> PC_out[31:0]	32	0	68

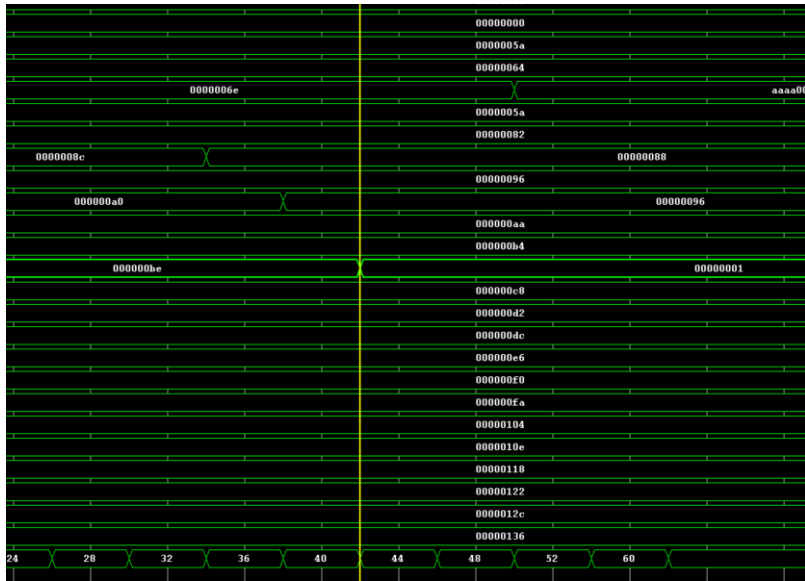For SLT, you can see that R19 changes to 1 because at that instruction $R17 < R18$ based on our testbench:




This happens at PC 40 because this is when we made it occur on the testbench.

 For LUI, the contents of immediate we put in the instruction are shifted 16 bits to the left and assigned it to register 11 as seen here in the waveform:



This occurs at PC 48 because this is when it is supposed to according to our testbench.

 For BNE, it branches from PC_out 52 to 56 which means it skips one instruction as we indicated in testbench



Here is a picture of instruction (PC) 56 being skipped, as the actual register values are irrelevant to testing this.

For J, it jumps from PC_out 60 to 68 which means it skips one instruction as we indicated in testbench:

